Dr. Jivraj N. Mehta Government Polytechnic, Amreli
ICT Department

Course: Fundamental of Electronics **Course Code: DI01000051**

ASSIGNMENT- 2

Unit – 2: Applications of Diodes and Rectifiers

CO: DI01000051.2. Develop different types of rectifiers using PN junction diode.

Sr. No	Question
1	Define Clipper and Give Classification of different types of clipper circuits.
2	Draw and explain positive clipper circuit with waveform.
3	Draw and explain Negative clipper circuit with waveform..
4	Draw and Explain Biased clipper with Waveform
5	Define following terms: 1) Rectifier 2) Ripple factor 3) Filter 4) PIV of a diode 5) Efficiency 6) transformer utilization factor
6	State why we Need rectifier Circuit? Give Classification of Rectifier in short
7	Explain working of Half wave rectifier with waveform
8	Explain working of full wave rectifier with two diodes.
9	Explain working of Full wave bridge rectifier with circuit diagram and wave form.
10	Compare Different types of Rectifier.
11	List application of Rectifier
12	Justify why filter circuit is required after rectifier?
13	List Different types of Filter circuit.
14	Explain working of Pi(π) type capacitor filter.